Task 4.1P Implement 16-bit register in HDL

- To build this 16-bit register, I used the Nand Tetris hardware simulator's HDL programming.
- 16 single-bit register arrays are formed to produce this.
- After that, joining them to create the 16-bit register.
- There is a DFF and a Mux in the 1-bit register.
- The chip interface is made up of an output pin that outputs the cell's current state, an input pin that carries a data bit, and a load bit that allows the cell to be written to.
- After that, in order to fully implement the 16-bit register, I had to construct 16 arrays of 1-bit registers and connect them to one another in the 16-bit register HDL file.
- Using bus syntax, the in [0] and out [0] bits are connected, and this connection process is repeated up to the 16th bit. To put it another way, bus syntax links the input bit in [0] to the output bit out [0], and this connection is maintained progressively up to the 16th bit.
- After that, launch the Hardware Simulator and load the test file and 16-bit register HDL file.
- The comparison concluded satisfactorily, demonstrating the successful creation of a 16-bit register.



